



Lakshya JEE (2024)

Electromagnetic Induction


DPP-08

- The time constant of $L - R$ circuit is doubled if _____.
 - Both L and R become two times
 - L becomes four times and R becomes two times
 - L becomes two times and R becomes four times
 - L becomes two times and R becomes eight times
- A solenoid of resistance 50Ω and inductance 80 Henry is connected to a 200 V battery. How long will the current take to reach 50% of its final equilibrium value?
 - 1.109 sec.
 - 1 sec.
 - 2 sec.
 - 1.5 sec.
- In an LR circuit current at $t = 0$ is 20 A. After 2 s it reduces to 18 A. The time constant of the circuit is (in second) _____.
 - $\ln\left(\frac{10}{9}\right)$
 - 2
 - $\frac{2}{\ln\left(\frac{10}{9}\right)}$
 - $2\ln\left(\frac{10}{9}\right)$
- In the given circuit find the ratio of i_1 to i_2 . Where i_1 is the initial (at $t = 0$) current, and i_2 is steady state (at $t = \infty$) current through the battery _____.

 - 1.0
 - 0.8
 - 1.2
 - 1.5
- In a series $L - R$ growth circuit, if maximum current and maximum induced emf in an inductor of inductance 3mH are 2A and 6V respectively, then the time constant of the circuit is _____.
 - 1 ms
 - $1/3$ ms
 - $1/6$ ms
 - $1/2$ ms
- The battery shown in the figure is ideal. The values are $\varepsilon = 10$ V, $R = 5\Omega$, $L = 2\text{H}$. Initially the current in the inductor is zero. The current through the battery at $t = 2$ s is _____.


 - 12 A
 - 7 A
 - 3 A
 - None of these
- An ideal coil of 10 H is joined in series with a resistance of 5Ω and a battery of 5 V. 2 s after joining, the current flowing in ampere in the circuit will be _____.
 - e^{-1}
 - $(1 - e^{-1})$
 - $(1 - e)$
 - e
- An $L-R$ circuit has a cell of emf E , which is switched on at time $t = 0$. The current in the circuit after a long time will be _____.
 - Zero
 - $\frac{E}{R}$
 - $\frac{E}{L}$
 - $\frac{E}{\sqrt{L^2 + R^2}}$

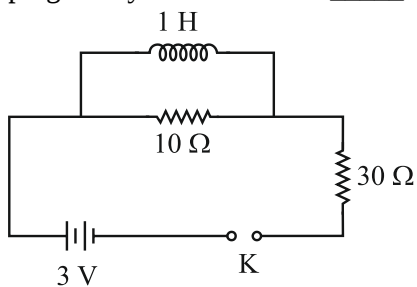9. In figure, final value of current in 10Ω resistor, when plug of key K is inserted is _____.



- (1) $\frac{3}{10}A$ (2) $\frac{3}{20}A$
 (3) $\frac{3}{11}A$ (4) zero

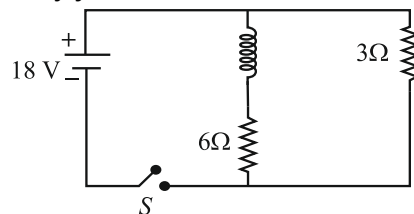10. In the following circuit the value of current i through the battery just after the switch S is closed is



- (1) 3 A (2) 6 A
 (3) 2 A (4) 9 A



Note: Kindly find the Video Solution of DPPs Questions in the DPPs Section.

Answer Key

1. (2)
2. (1)
3. (3)
4. (2)
5. (1)

6. (1)
7. (2)
8. (2)
9. (4)
10. (2)



PW Web/App - <https://smart.link/7wwosivoicgd4>

Library- <https://smart.link/sdfez8ejd80if>